

LAB 3

1. 8 x 3 Priority Encoder using concurrent statements
2. Use concept of array and with select statement to design ROM which implements the

following functions:

$$F1 = A'BC + AB + A'BC'$$

$$F2 = ABC' + A'B'C' + A'C$$

$$F3 = ABC + AB'C' + A'B'C$$

$$F4 = AB + BC + CA$$

3. Design a T latch using
 - (i) Concurrent Statement
 - (ii) Sequential StatementsNote: First design without any delay and simulate design (Identify the problem) then add delay of 3ns and verify the simulation results
4. Design D Flip Flop with
 - (i) Asynchronous Reset
 - (ii) Synchronous Reset
 - (iii) Asynchronous Reset and Preset.
 - (iv) Asynchronous Reset and Preset with Enable.
5. Ring Counter (6-bits) using Schematic. Verify following frequency dividers $f/6$, $f/3$ and $f/2$ using concept of generic.